



Figure 1

A stepper-motor controller requires only a few logic circuits.

NOTES: IC₁: SN74HC86.
IC₂: SN74LS76A.