



**Figure 3**

The complete stepper-motor controller uses a DDS IC to generate the variable frequencies for the circuit in Figure 1.