



**Figure 1**

Combining two opposite-polarity power supplies can increase the available power from a flyback regulator.