



**Figure 5**

Placing a flip-flop inside the driver and using a lowpass filter in the receiver help minimize signal skew and reduce noise from the pc board.