



**Figure 2**

**This circuit provides fault protection and digital-signal recovery for a 4- to 20-mA current loop.**