



**Figure 1** You can use cross-coupled differential transistor pairs as current-mode switches.