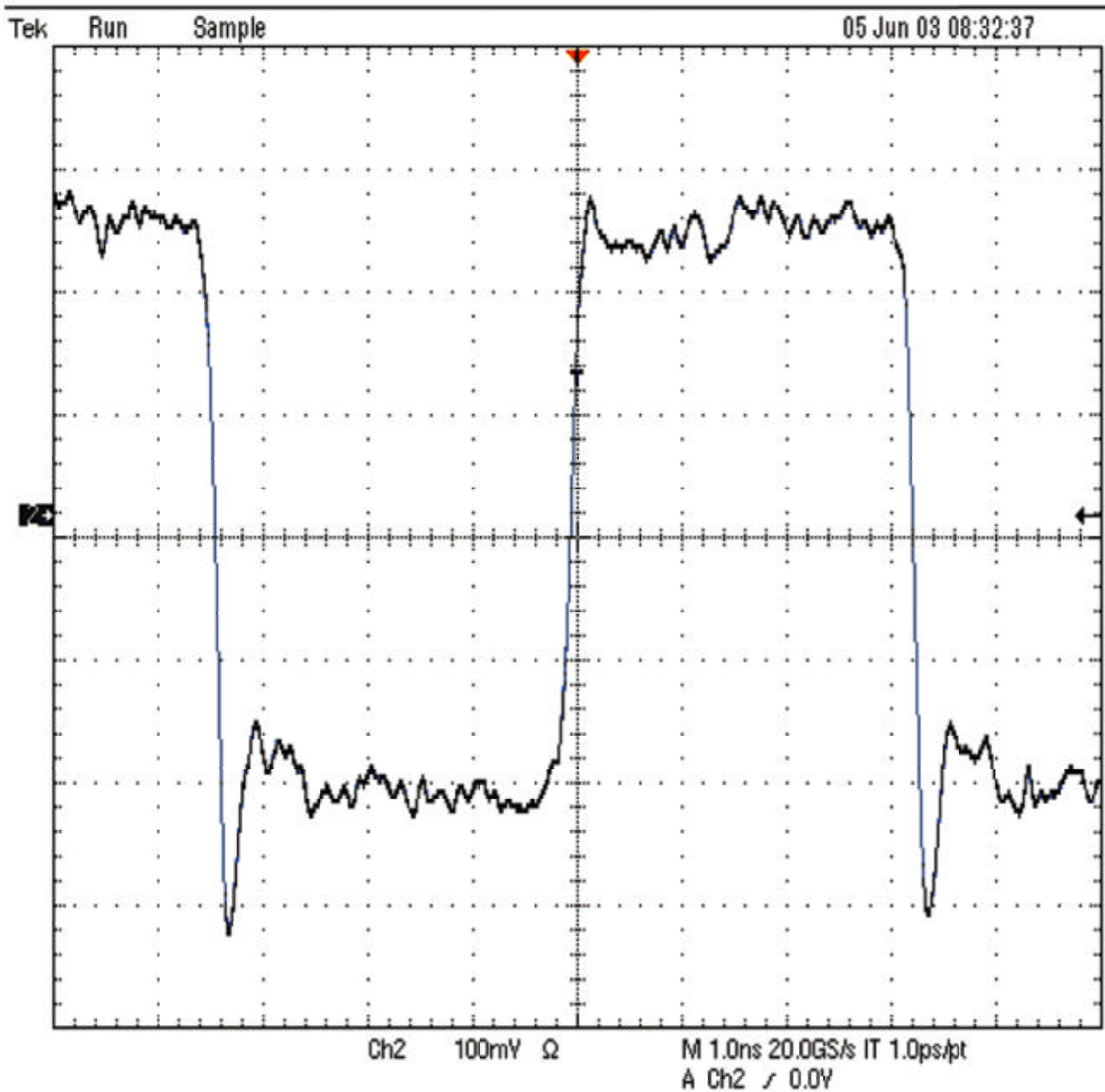


Figure 3



The circuit in Figure 2 produces outputs with less-than-200-psec rise and fall times.