



Figure 1

To build an analog filter, you can use an RC lowpass filter (a), an active lowpass filter (b), or a switched-capacitor lowpass filter (c).