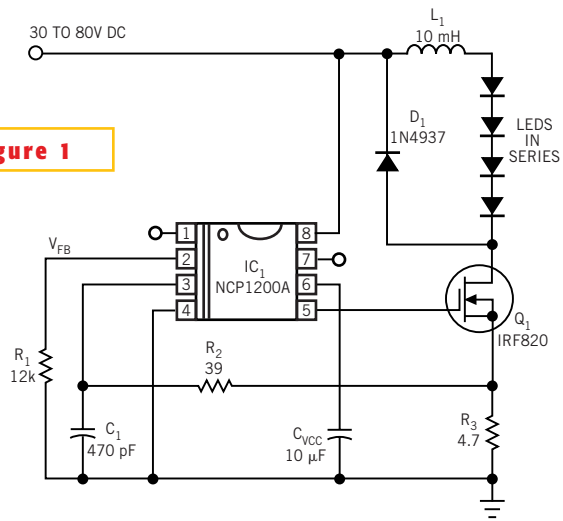


**Figure 1**



**A high-voltage controller makes an ideal off-line LED driver.**