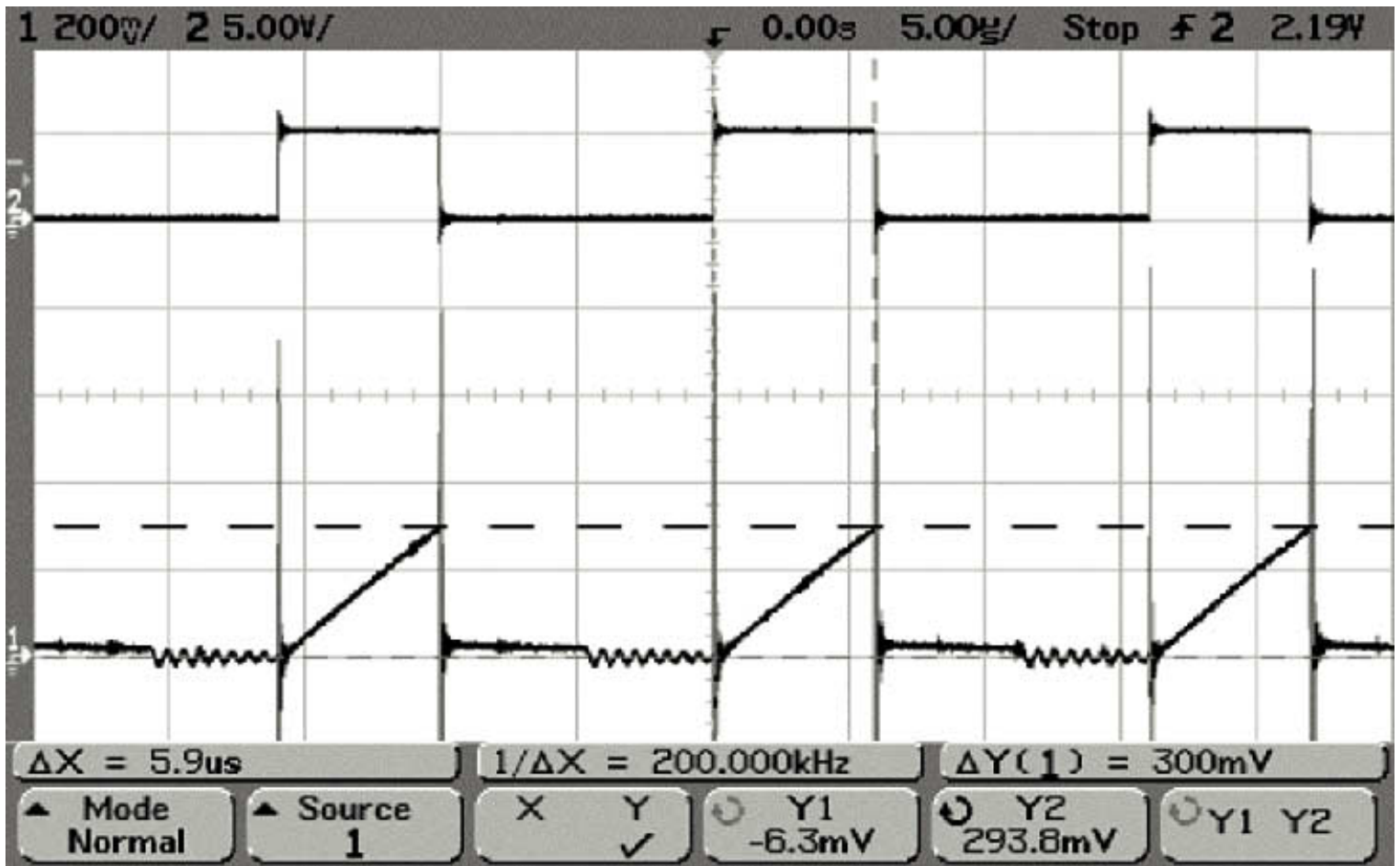


Figure 4



A working example of the boost converter implementing the basic topology of Figure 1 shows the duty cycle (top) and the current-ramp-down waveform (bottom) for the circuit in Figure 1.