



**Figure 2**

The generalized gain-cell model includes the amplifier's input-referred voltage- and current-noise sources, and a noise voltage corresponding to the signal-source impedance.