



Figure 1

Using MOSFETs instead of a diode for reverse-battery protection prevents inductive-kick problems in motor-drive circuits.