



Figure 1

By repeatedly charging a storage capacitor and then dumping its charge into a small motor, this circuit can run the motor on only 10 nA of current.