



Figure 1

This circuit configuration turns off unneeded LEDs when it's dark.