



Figure 2

In this circuit, the MOSFET's drain waveform generates the demagnetization signal for the controller IC.