

Edited by Bill Travis

Positive feedback yields fast amplifier with precision dc offset

Steve Woodward, Chapel Hill, NC

SOME SIGNAL-PROCESSING applications require a high-speed, low-noise, dc-coupled amplifier that incorporates a precision dc-offset adjustment. Examples include oscilloscopes, in which the offset adjustment typically acts as a “position” control), ADC-input gain blocks, and scanning-beam-microscopy deflection circuitry. **Figure 1** illustrates the circuit concepts. Op amp IC_{2A} is a 70-MHz, high-slew-rate device configured with a fixed gain of 3 (9.5 dB) and a $\pm 10\text{V}$ precision offset adjustment. Op amp IC_{1A} buffers and thereby linearizes the offset potentiometer. IC_{1A} is a low-cost, low-fre-

quency device that befits the dc circuit it occupies. But the mismatch between the frequency responses of IC₂ and IC_{1A} creates the need for the novel topology of **Figure 1**. An obvious way to couple IC_{1A} and IC_{2A}, which might seem to allow the addition of dc offset, would be to omit R₁, R₂, R₃, and C₁ and simply connect IC_{1A} as a unity-gain buffer providing the termination for the gain-set resistor, R₃. Unfortunately, this scheme wouldn't work, because the output impedance of the pokey IC_{1A} starts rising at frequencies far below the capabilities of the speedy IC₂. This drawback would ruin the high-frequency performance of the composite

Positive feedback yields fast amplifier with precision dc offset.....91


Buck regulator forms high-power, inverting -5V supply92

Low-loss circuit powers solar lantern94

RC network quashes auxiliary winding in quasiresonant converter.....98


Low-power CMOS oscillator has push-pull output100

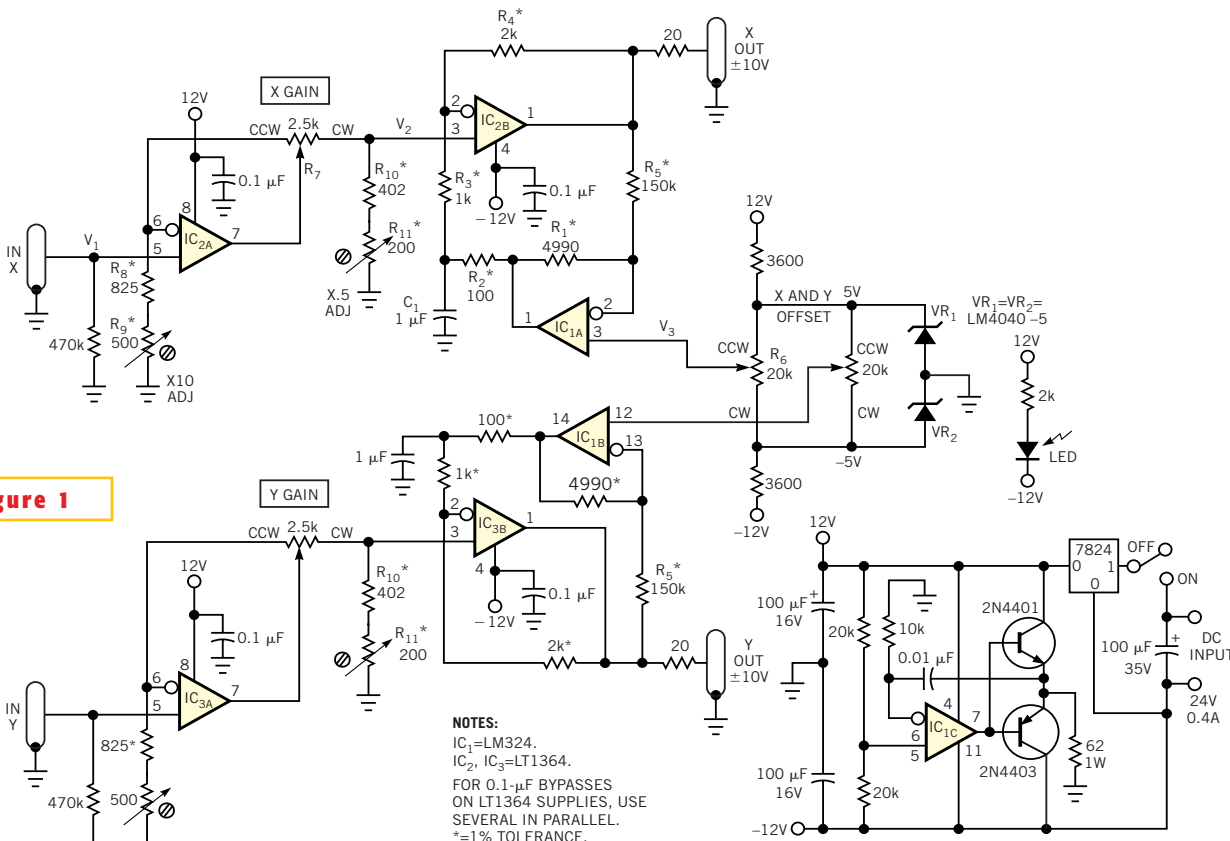Publish your Design Idea in EDN. See the What's Up section at www.edn.com.




In this circuit, positive feedback makes it possible to obtain wide-range dc offset without compromising bandwidth.

Figure 2

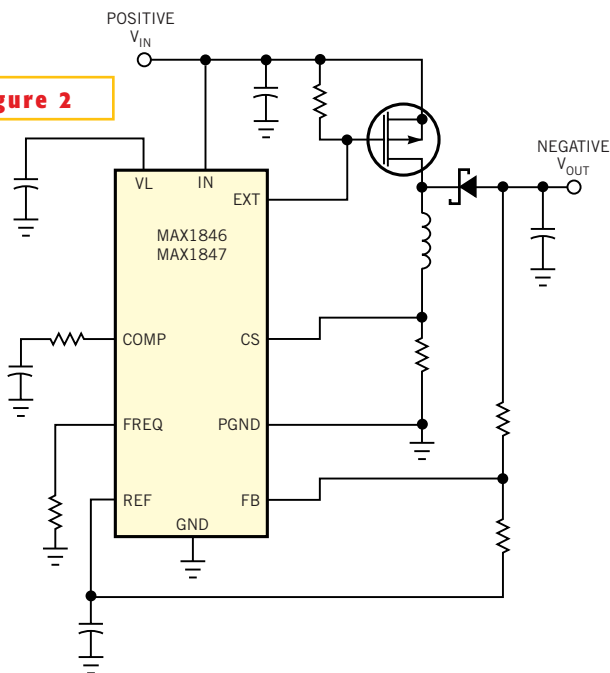

This conventional inverting power supply uses a relatively inefficient p-channel MOSFET.

Figure 3

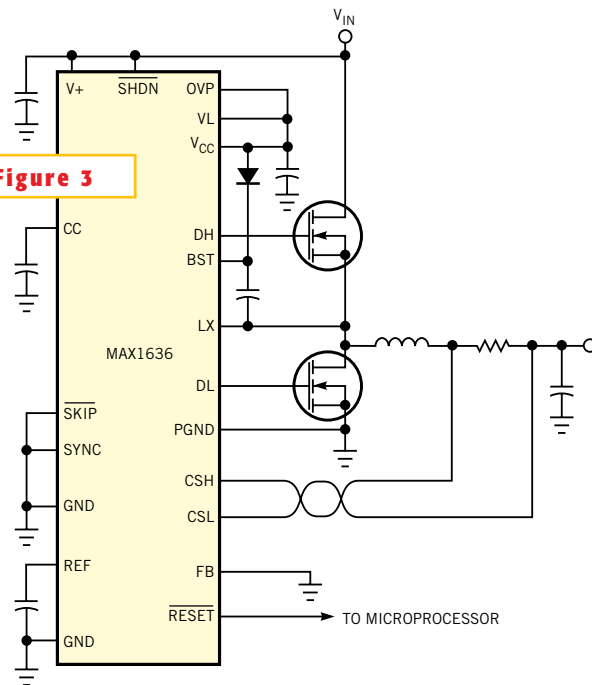

IC₁ in Figure 1 normally operates as a high-power buck converter.

configuring a high-power buck converter, IC₁ as an inverter, thus exploiting an all-n-channel design. Efficiency is 90% with a 12.35V input, -5.02V output, and 4.7A load. The efficiency is 84% with a 4.56V input, -5.02V output, and 3.3A load. You can easily accommodate -5.2V applications by changing the values of R₁ and R₂. (Operation at -5.2V incurs a

small penalty on maximum output current.) Input and output ripple voltages directly relate to the input and output capacitors' ESR (equivalent series resistance), so you should carefully select these capacitors. Circuit layout is also extremely important, as for all dc/dc converters. You may want to consider the

(www.maxim-ic.com). The kit includes a small pc board with optimized layout and all components necessary for operating the MAX1636. Because the board's layout is similar to the one required in Figure 1, the kit can serve as a rough layout guide for this Design Idea. □

Low-loss circuit powers solar lantern

Ramsesh Kumar, Bangalore, India

THE SOLAR-LANTERN CIRCUIT in Figure 1 is a low-loss configuration that uses a 7W, four-pin CFL (compact fluorescent lamp) and a 12V, 7-Ahr, sealed, maintenance-free battery. The inverter features greater-than-85% efficiency, less-than-2-mA quiescent current, and a shunt-charge controller with deep-discharge and overcharge protection for the battery. The low quiescent current and the deep-discharge and overcharge protection ensure long life for the battery. The preheating feature in the inverter avoids the blackening of the end of the CFL, thereby ensuring long life. The circuit finds application in rural areas

as a reliable, compact, portable light source and in urban areas as an emergency-lighting system. The shunt charge-controller circuit comprises IC₁, a low-current, voltage-reference 2.5V LM385, and IC₂, an LM324 comparator. IC_{2A}, with resistors R₁ through R₈ and transistor Q₁, provides protection against deep discharge of the battery.

The circuit switches off the load, including the inverter and the lamp, when the battery voltage falls below 10.8V and thus protects the battery from deep discharge. Under a no-

load condition, the discharged battery voltage is approximately 12.2V. Hence, the circuit provides a deep-discharge reset level of 12.3V to avoid oscillations. Red LED₁ indicates a low-battery condition. IC_{2B} with resistors R₉ through R₁₄ and transistor Q₂ provides protection against overcharging the battery. Q₂ switches on

TABLE 1—WINDING DETAILS FOR TRANSFORMER

Start pin	End pin	Wire gauge	Turns	Inductance
2	1	26	21	28 mH
3	4	26	21	28 mH
6	10	38	380	17 mH

Core: EE25/13/7

and shunts the solar array when the battery voltage exceeds 14.8V and thus protects the battery from overcharging. Q_2 turns off when the battery voltage drops below 12.5V and thus enables battery charging. D_2 is a reverse-blocking diode. It prevents the discharge of the battery through the solar cells when the cells are not generating electricity. Amber LED₂ indicates that the battery is in full-charge

condition. Green LED₃, along with IC_{2C} and resistors R_{15} through R_{20} , provides an indication of charging.

Tables 1, 2, and 3 give core and winding details for the magnetic components in the circuit. The inverter uses a Class D, push-pull, force-driven topology with MOSFETs as switching devices. IC₃, an SG3524, drives the inverter. The force-driven topology ensures trouble-free start-up in all environmental conditions. The switching frequency is approximately 26

kHz. Q_6 , along with resistors R_{29} , R_{30} , and R_{31} and capacitor C_{10} , forms the pre-heating circuit. In addition to the 12V, 7-Ahr sealed, maintenance-free battery, the circuit uses a 10W, 12V single-crystalline-silicon solar-cell panel. The recorded backup time is approximately eight to 10 hours for a fully charged battery with a light output of 370 lumens using a 7W, four-pin CFL. □

TABLE 2—WINDING DETAILS FOR INDUCTOR L₂

Start pin	End pin	Wire gauge	Turns	Inductance
1	2	27	215	8.2 mH

Core: EE25/13/7

TABLE 3—WINDING DETAILS FOR INDUCTOR L₁

Wire gauge	Turns
26	100

Core: Ferrite rod, 5-mm diameter, 25 mm long.

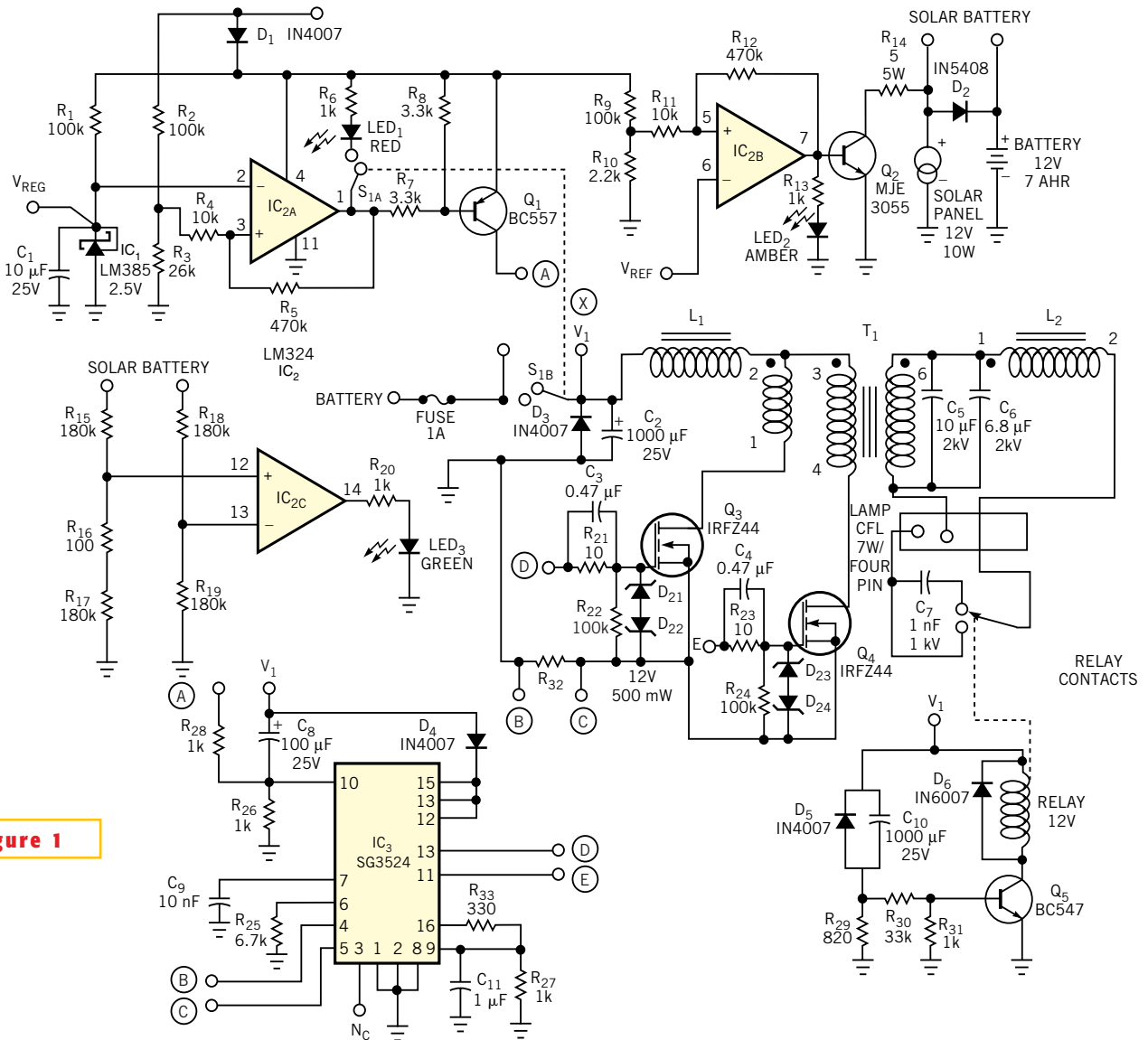


Figure 1

This solar-powered lantern driver can serve as an emergency lighting system.

RC network quashes auxiliary winding in quasiresonant converter

Nicolas Cyr, On Semiconductor, Toulouse, France

QUASI-SQUARE-WAVE-RESONANT converters, also known as QR (quasiresonant) converters, allow the design of flyback-type SMPSs (switch-mode power supplies) with a reduced EMI (electromagnetic-interference) signature and improved efficiency. You can achieve so-called QR operation by authorizing the turn-on of the switching MOSFET when the drain voltage reaches its minimum—hence, the name valley switching operation. The circuit usually externally detects the minimum drain voltage of an auxiliary winding, which delivers a voltage image of the core’s internal flux activity. The circuit in **Figure 1** offers a solution that incorporates core-reset detection with the aid of an auxiliary winding. As you can see, the auxiliary winding solely performs the function of core-reset detection. To further simplify this schematic, you can remove the auxiliary winding and use the drain signal itself to generate the demagnetization signal that Pin 1 of the NCP1207 requires. **Figure 2** shows this arrangement. Thanks to its use of high-voltage technology, On Semiconductor’s (www.onsemi.com) NCP1207 QR controller can derive its power directly from the rectified mains via its “dynamic-self-supply” feature.

Capacitor C_1 removes the dc component of the drain signal. R_1 , together

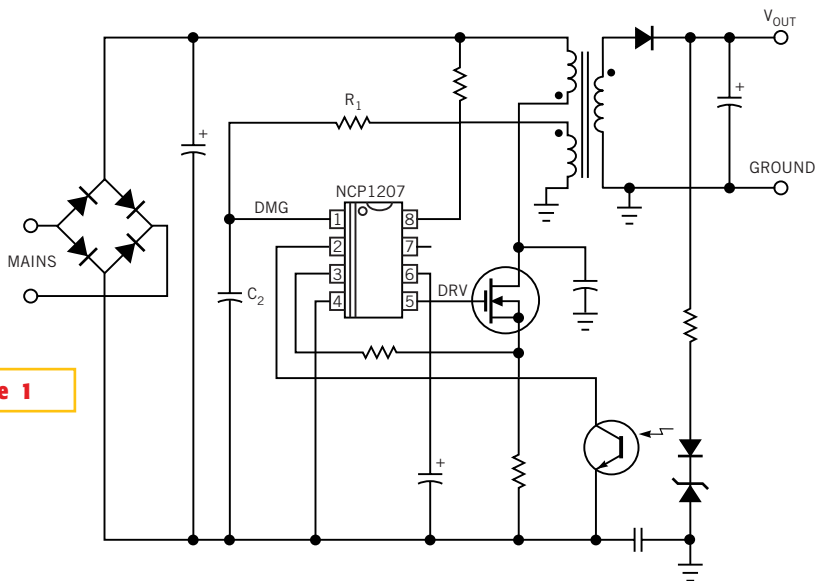


Figure 1

In this configuration, an auxiliary winding performs the function of core-reset detection.

with the internal resistor on the NCP1207 demagnetization pin (Pin 1), creates a resistor divider. The divider safely limits the voltage you apply on the controller when the drain swings high. C_2 delays the signal to detect exactly the drain signal valley. Compared with **Figure 1**, where R_1 and C_2 were present, the only addition is C_1 (in replacement of the auxiliary winding). Because capacitor C_1 touches the MOSFET drain, it must sustain at least the same maximum voltage: A 220-pF, 1-kV or 1-nF, 1-kV ceramic capacitor perfectly fills the bill. The internal resistance of NCP1207’s demagnetization pin is 28 k Ω . The value of R_1 ranges from 1 to 2 M Ω if you want to create a 5V signal with a maximum drain voltage of 600 and 900V. The value of capacitor C_2 depends on the frequency of the resonating network comprising the primary inductance, L_{PRI} , and the total capacitance of the drain node. You adjust the values of R_1 and C_2 directly on the board to reach the

best valley detection possible. Because R_1 has a relatively high value, it is essential that the component resides close to the controller’s Pin 1. The **Figure 3** waveforms show the final application results. The waveforms are captured on a single-output, 30W SMPS delivering 16V. In this application, $C_1=220$ pF/1 kV, $R_1=1.5$ M Ω , and $C_2=100$ pF. By properly adjusting the time constants, you can obtain perfect valley switching. □

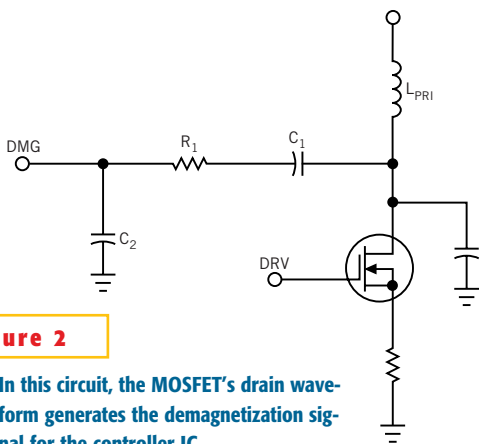


Figure 2

In this circuit, the MOSFET’s drain waveform generates the demagnetization signal for the controller IC.

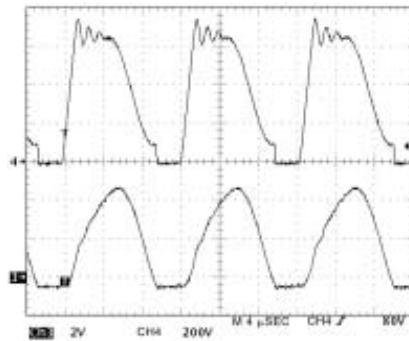


Figure 3


These waveforms illustrate the operation of **Figure 1**’s circuit without the auxiliary winding.

Low-power CMOS oscillator has push-pull output

Shyam Sunder Tiwari, Sensors Technology Private Ltd, Gwalior, India

DIGITAL OSCILLATORS often generate TTL- or CMOS-level outputs, referred to ground. Generating a symmetric bipolar output with respect to ground presents a challenge. In this design, four 1.5V flashlight cells create $\pm 3V$ voltage sources, and the midpoint of cells acts as the ground reference (**Figure 1**). The oscillator at the input, based on the R_1C_1 time constant, generates a $\pm 2.8V$ bipolar output. The symmetrical output waveform requires no dc-blocking capability to drive a piezoelectric buzzer or loudspeaker. The circuit works well with ± 1 to $\pm 3V$ sources and delivers a symmetrical output over the full range of source voltages. □

Figure 1

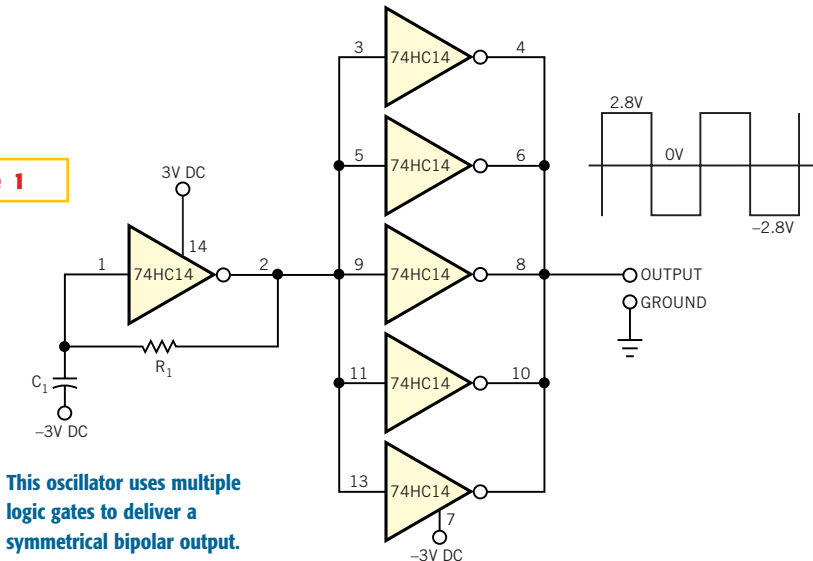

This oscillator uses multiple logic gates to deliver a symmetrical bipolar output.