



**Figure 3**

NOTE:  $V_{TN}$  = NMOS-THRESHOLD VOLTAGE (1.5V).

The voltages and MOSFET states appear like this during a positive-overvoltage event.