



Figure 5

In this circuit, the ADG466 channel protector guards the sensitive inputs of an instrumentation amplifier from a sensor fault.