



Figure 1

Using a simple CMOS IC, this flyback power-supply circuit exhibits extremely low noise.