



Figure 1

A simple circuit produces $\pm 5V$ from a single positive input without the need for a transformer.