



Figure 3

Adding a driver/power switch to Figure 2 permits partial capacitor discharge, allowing pulsed low-level light before main flash, thus minimizing "redeye" phenomena.