



Figure 1

Adding a current-mirror circuit to a boost circuit allows you to get just enough boost voltage.