



Figure 1

This simple circuit provides positive-output voltage LCD drive.