



Figure 1

This circuit provides ideal bias for an ISFET, a sensor used to measure fluid acidity.