



Figure 1

This simple circuit uses a microprocessor supervisor and a shunt regulator to form an over-voltage/undervoltage-protection circuit.