



**Figure 1**

A hysteretic switching controller can do double duty as an overvoltage-protection circuit.