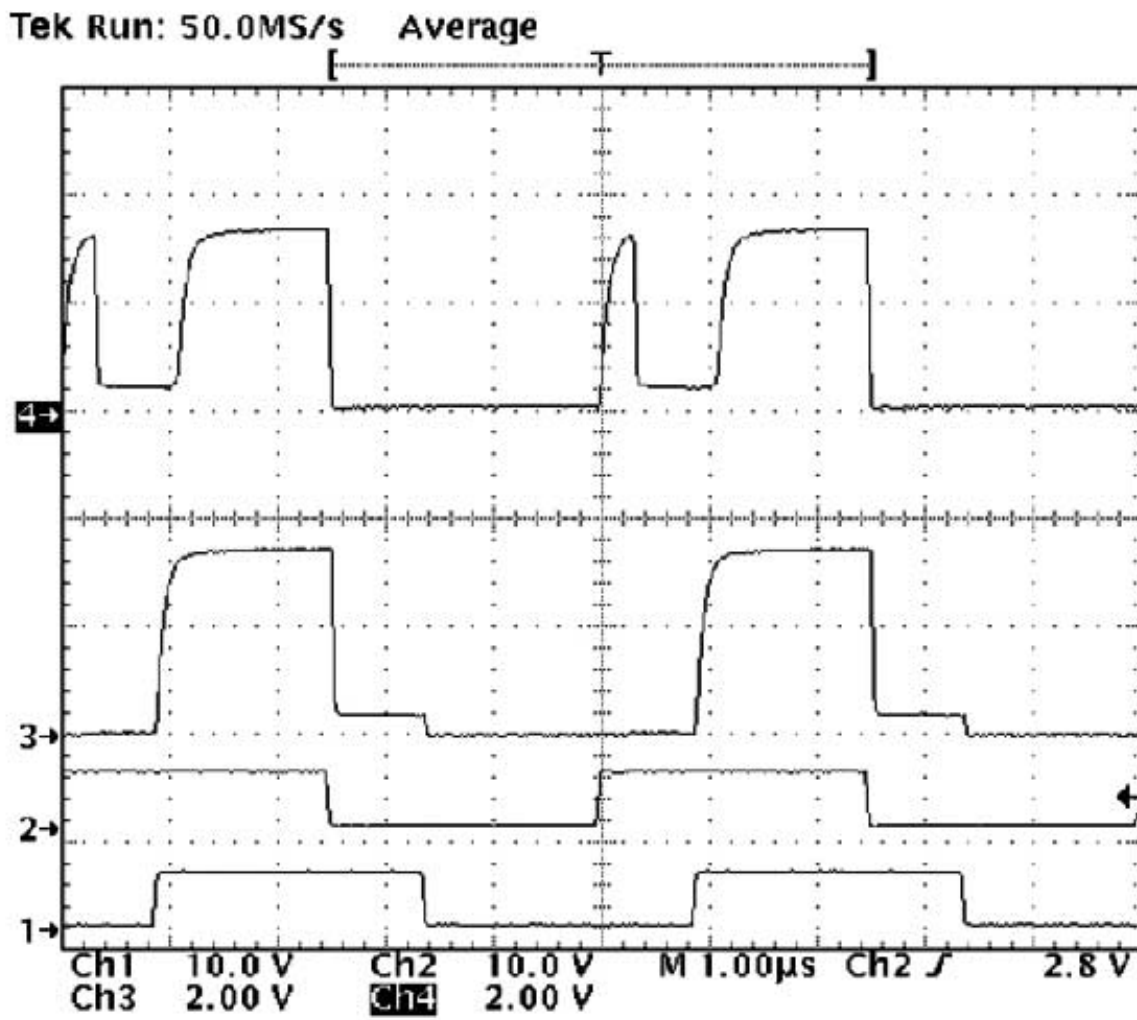


Figure 2



The simple I²C isolator produces large glitches under some circumstances.