



**Figure 1**

This four-IC circuit uses no transformers and converts 12V to 180V, using off-the-shelf components.