



**Figure 1**

This motion-detector circuit works with 6V battery voltages that sag as low as 2V.