



Figure 1

This inexpensive power supply uses a preregulator to boost efficiency.