



**Figure 1**

This circuit enables a 36V current-monitoring IC to operate at common-mode voltages as high as 130V.