



**Figure 1**

This charge-pump circuit uses analog switches to achieve ultralow quiescent current.