



**Figure 3**

For USB applications requiring 5V, this circuit provides precise inrush limiting.