

**Figure 1**

This circuit monitors dc voltage on a phone line and presents 10-M $\Omega$  leakage resistance across the line.

