



**Figure 1**

This simple circuit level-shifts ac signals to accommodate the  $\pm V_s$  supplies.