



Figure 2

An added series resistor makes this circuit's switching frequency more predictable.