



**Figure 1**

You can use slow diodes to generate dead time in a half-bridge configuration.