



**Figure 2** A logic inverter cleans up the pseudo square wave (top) from the flying capacitor; the result (bottom) is a stable clock source for the microcontroller.