



**Figure 1**

A digital potentiometer makes it easy to adjust  $V_{COM}$  to the desired value.