



Figure 1

A power-MOSFET gate driver does double duty as negative-supply power switch.