



Figure 4

This circuit senses the magnitude of a positive supply and turns on a negative supply when the positive supply exceeds a threshold.