



Figure 5

The circuit in Figure 4 turns on the negative supply when the positive supply exceeds 1.5V.