



NOTE:
 SET VOLTAGE AT TP₁ TO TWICE Q₁'S V_{GS(OFF)},
 SO THAT $0.50V_{GS(OFF)} = 0.7RC = 150 \text{ mSEC}$.

Figure 1

This simple circuit provides soft muting for line-level audio circuits.