



Figure 2 You amplify the ΔV_{BE} and add it to a pnp transistor for V_{BE} to form a bandgap voltage reference.