



Figure 3

A multichannel Class D amplifier (a) can minimize transient current demand from the power supply if you introduce phase shift in the PWM signal (b).