



**Figure 1**

A two-IC circuit allows signal level-shifting in both directions; signal-flow direction is under circuit control.