



Figure 1

You can use a simple ferrite-bead transformer to isolate logic-level signals.