



Figure 1

A basic gain-programmable amplifier circuit uses digital outputs from a microcontroller to set gain.