



**Figure 1** You reduce noise with an  $R_1C_1$  filter, but the filter introduces an error due to output current flowing through  $R_1$ , so reducing this current requires a buffer.