

Edited by Brad Thompson

## Dual-output nonisolated SMPS powers appliances

Fabio Cacciotto, STMicroelectronics, Catania, Italy

**M**ODERN APPLIANCES offer a range of features that rely heavily on microcontrollers and auxiliary circuits. Although conventional iron-core transformers can provide ac line-isolated, low-voltage power for a microprocessor, coupling the processor's control signals to line-side power switches requires yet another layer of electrical isolation, such as optocouplers or pulse transformers.

Designers can avoid the complexity and expense of adding isolation components by powering the microcontroller and its auxiliary circuits from the non-isolated ac line. An offline SMPS (switched-mode power supply) can easily produce a single low voltage, but obtaining multiple voltages can prove more challenging and require a relatively complicated design.

As an alternative, you can use a single-


chip SMPS controller, such as STMicroelectronics' Viper22A, IC<sub>1</sub>, to derive as much as 3.3W of regulated dual-voltage power over an ac line-voltage range of 88 to 265V ac (**Figure 1**). For the values in the figure, this circuit delivers  $-5V \pm 5\%$  at currents as high as 300 mA and  $-12V \pm 10\%$  at currents as high as 150 mA.

The Viper22A's internal circuitry includes a 60-kHz clock oscillator, a voltage reference, overtemperature protection, and a high-voltage power MOSFET that can provide several watts of power. Although the Viper22A occupies an eight-lead package, operating requires only four connections: operating power, V<sub>DD</sub>; feedback, FB; and the MOSFET's source and drain. The remainder of the pins, redundant source and drain connections, help dissipate heat into the pc board.

Resistor R<sub>4</sub> limits input surge current

Dual-output nonisolated SMPS powers appliances .....	99
High-voltage amplifier drives piezo tubes .....	100
Phone wire, RJ-11 jacks and optocouplers build a bus .....	101
Use a PC's parallel port to program a clock source .....	102
Constant-on-time buck-boost regulator converts a positive input to a negative output .....	104
Rainbow LED indicates voltage with color .....	106
<b>Publish your Design Idea in EDN. See the What's Up section at <a href="http://www.edn.com">www.edn.com</a>.</b>	

and doubles as a protective fuse. Diode D<sub>1</sub> rectifies the ac line voltage, providing approximately 160V dc to a filter comprising C<sub>1</sub>, R<sub>1</sub>, L<sub>1</sub>, and C<sub>2</sub>. In addition to smoothing dc ripple, the filter reduces

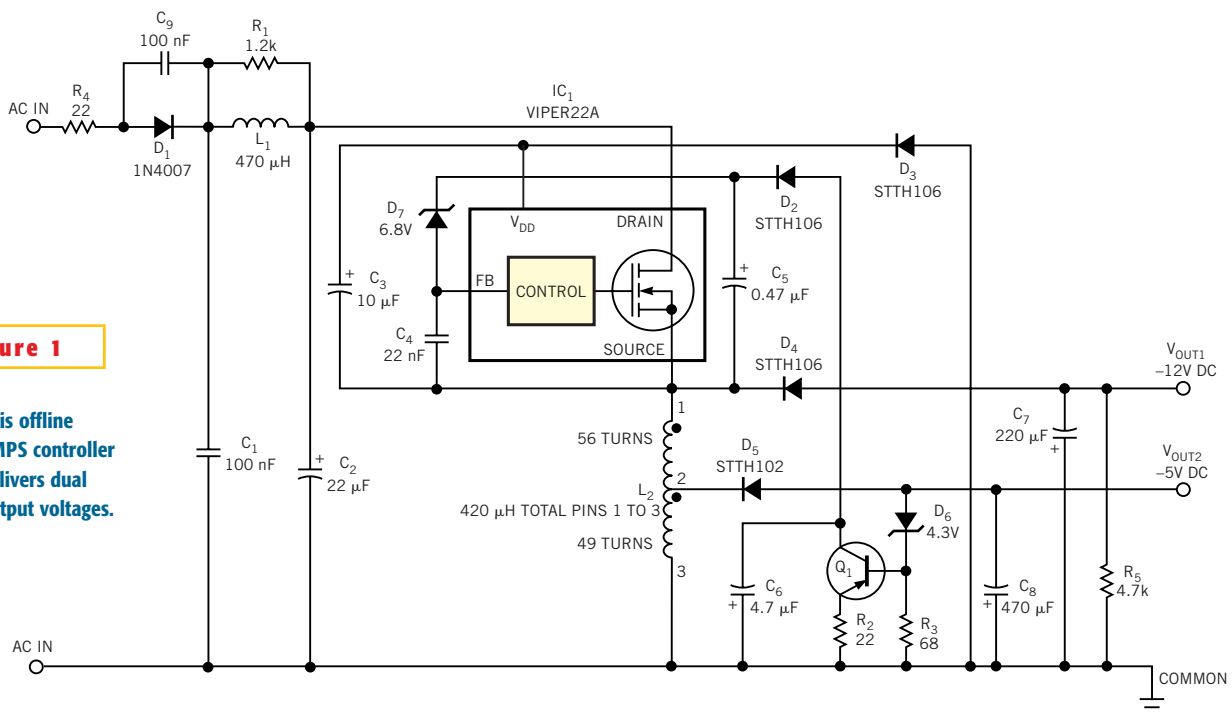

**Figure 1**

This offline SMPS controller delivers dual output voltages.

electromagnetic interference to help achieve compliance with EU standard 55014 CISPR14. Snubber capacitor  $C_9$  across  $D_1$  helps further reduce conducted emissions.

Reservoir capacitor  $C_3$  acquires a positive charge via diode  $D_3$  during the MOSFET's off-time and supplies  $V_{DD}$  to  $IC_1$  during the MOSFET's on-time. Reverse voltage across  $D_3$  can reach the sum of the peak rectified line voltage plus the

magnitude of the maximum regulated dc output voltage, so use a fast-recovery diode rated for 600V peak-inverse voltage for  $D_3$ .

The voltage at  $V_{OUT2}$  provides feedback to close the regulation loop. The sum of general-purpose PNP transistor  $Q_1$ 's base-emitter voltage plus  $D_6$ 's reverse voltage sets  $V_{OUT2}$  at  $-5V$ . Zener diode  $D_7$  shifts the voltage at  $IC_1$ 's feedback input terminal into its linear range (0 to 1V).

To avoid high-frequency instability in the compensation loop, keep connections to ceramic capacitor  $C_4$  as short as possible. Inductor  $L_2$  comprises a TDK SRW0913 ferrite drum core with two windings whose turns ratio sets the output voltage at  $V_{OUT1}$ . To maintain regulation when  $V_{OUT1}$  is unloaded and  $V_{OUT2}$  is fully loaded, add bleeder resistor  $R_5$  from  $V_{OUT1}$  to common ground. □

## High-voltage amplifier drives piezo tubes


Bipin Duggal, Netaji Subhas Institute of Technology, New Delhi, India

**P**IEZOELECTRIC TUBULAR positioners that drive manipulators in scanning tunneling microscopes require high-voltage, low-current drive circuits. The circuit in **Figure 1** can drive high-resistance, low-capacitance piezoelectric loads at a  $-3$ -dB bandwidth of 6 kHz. It offers a low-cost alternative to commercial drivers. Transistors  $Q_3$  and  $Q_4$  form a current mirror, with  $R_3$  setting  $Q_4$ 's collector current as the following equation determines:  $I_{C3}=I_{C4}=[V_{CC}-(-V_{CC})-V_{BE}(Q_4)]/R_3$ . Operational amplifier  $IC_1$  provides base drive to  $Q_5$ , which in turn drives  $Q_6$ . With no signal applied to  $IC_1$ 's input, the collector currents of  $Q_6$  and  $Q_3$  balance, and the output taken from the junction of emitter followers  $Q_1$  and  $Q_2$  rests at 0V.



Applying an input signal to  $IC_1$  drives its output toward the positive or the negative 12V supply rail. Allowing  $IC_1$ 's output to saturate would introduce sufficient slew-rate delay to cause oscillations. Although specifying a relatively fast operational amplifier, an LF411, improves the amplifier's bandwidth and slew rate, antiparallel diodes  $D_1$  and  $D_2$  improve stability by restricting  $IC_1$ 's output excursion to one diode forward-voltage drop.

You can adjust  $R_7$  to minimize output dc offset voltage and slew rate. As a rule of thumb, select resistor  $R_7$  to be twice the value of  $R_9$ . The ratio of  $R_9$  to  $R_8$  sets the amplifier's gain. **Figure 2** shows the input and output waveforms using optimal values for  $R_7$  and  $R_9$ . Note that the  $V_{CEO}$  ratings for  $Q_1$  and  $Q_2$  limit  $V_{CC}$  and  $-V_{CC}$  to 300V or less. □

**Figure 1**

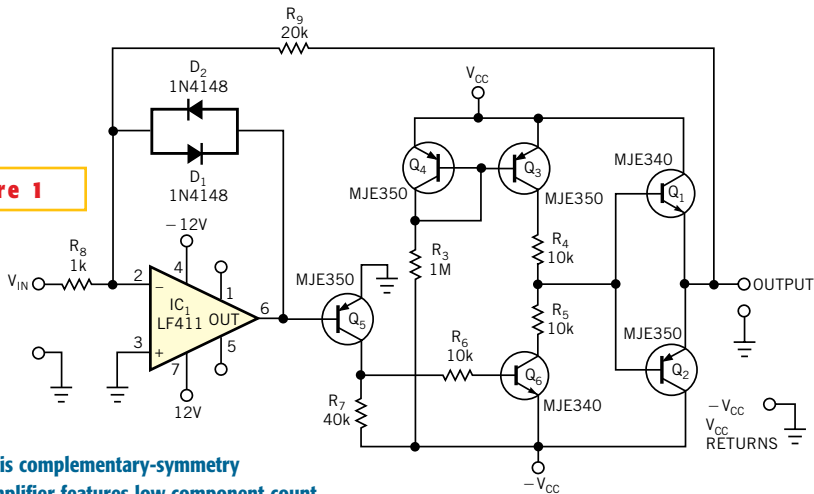

This complementary-symmetry amplifier features low component count.

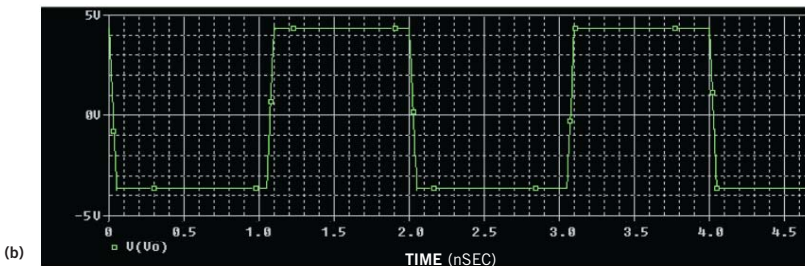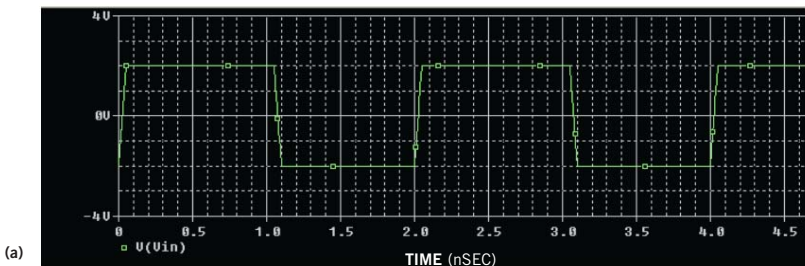

**Figure 2**

The input waveform shows input voltage applied as a pulse of  $-2$  to  $+2V$  (a). The output waveform shows an amplifier gain of 20 and minimized output offset (b).

# Phone wire, RJ-11 jacks and optocouplers build a bus

Ernie Deel, EFD Systems, Marietta, GA

**A**LTHOUGH CUTTING-EDGE technology reaps publicity, the real world often runs on modest hardware that's just "good enough" for home automation, alarm systems, and equipment-monitoring applications. **Figure 1** shows a low-speed, multidrop digital data network that uses inexpensive optoisolators, telephone jacks, and two-pair wiring.

This version of the familiar current loop offers a simplified and somewhat novel implementation in which optocouplers serve triple duty as level converters, isolation/protection devices, and bus interfaces. Galvanic isolation avoids ground loops, increases the effective


communications range, and adds a measure of protection for attached hardware.

However, inexpensive optocouplers introduce delays that can cause communications timing errors. Faster optocouplers can minimize errors at the expense of component cost and overall complexity, but using conservatively sized data packets at rates of 4.8 kbps or less allows the use of less expensive components. The H11A-817D optocouplers provide 5-kV isolation and current-transfer ratios of 300 to 600%.

A wall transformer/rectifier provides 12V-dc power for the isolated bus, and devices attached to the bus provide a few milliamperes of 5V power for commu-

nicating with isolated-side devices. You can implement RS-232, TTL, or inverted-TTL interfaces by configuring a single jumper and altering connections as appropriate. **Figure 1** illustrates representative examples of each interface.

When adding an RS-232 device, you can ensure compliance with the RS-232 standard by using a control line, such as DTR or RTS, to provide pull-up power, and negative voltage from the TX (transmit) line to passively pull the RX (receive) line low. You can devise a suitable master/slave-communication and error-detection protocol to meet your requirements. Using separate transmitter and

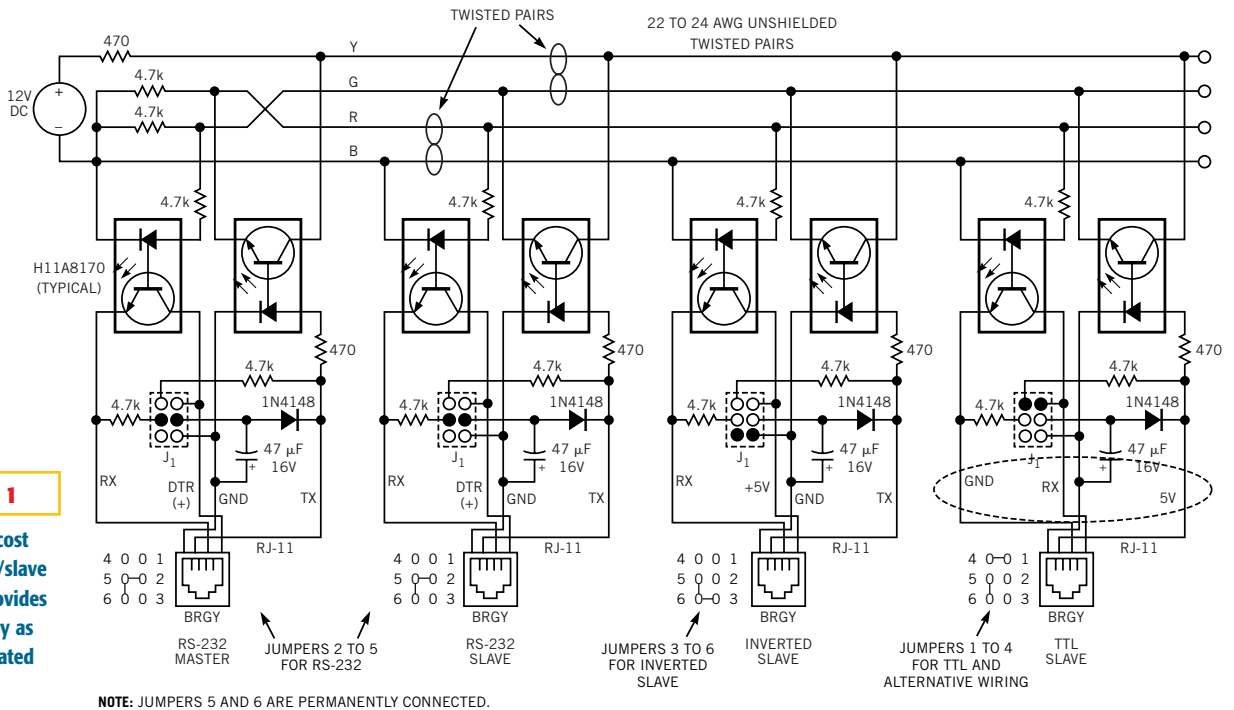

**Figure 1**  
A low-cost master/slave bus provides as many as six isolated nodes.

receiver lines helps simplify the required software. The node-point hardware easily fits inside an ordinary surface-mount

telephone jack, thus facilitating quick and easy RJ-11 hookups to master and slave devices. At a 4.8-kbps or lower data

rate, the bus can extend as far as 500 ft. Inexpensive dual twisted-pair telephone wire forms the bus. □

## Use a PC's parallel port to program a clock source


By William Grill, Honeywell BRGA, Lenexa, KS

**T**HIS DESIGN IDEA shows how you can use Linear Technology's LTC6903 programmable oscillator as a clock source for direct-digital synthesis, data conversion, switched-capacitor filtering, clock, and voltage-controlled oscillator circuits. The LTC6903 operates from 2.7 to 5.5V with modest power consumption and can produce clock signals at frequencies of 1 kHz to 68 MHz. Typical frequency error and resolution over the range are 1.1 and 0.1%, respectively.

You can control the programmable oscillator circuit in **Figure 1** via an IBM-compatible PC's parallel port, which also provides power to the circuit. Resistors  $R_1$  and  $R_2$  limit power-supply current drawn from parallel-port data bits  $DB_3$  and  $DB_4$ , and resistors  $R_3$  through  $R_5$  isolate programming bits  $DB_0$  through  $DB_2$ . A precision micropower voltage reference,  $IC_1$ ,

provides 4.096V of stable power to  $IC_1$  and  $IC_2$ . For optimal performance, minimize the lead lengths of bypass capacitors  $C_1$  and  $C_2$  with respect to  $IC_2$ 's power and ground connections. High-speed buffer  $IC_3$  isolates  $IC_2$ 's output and prevents frequency pulling due to load variations. **Listing 1** on the Web

version of this Design Idea at [www.edn.com](http://www.edn.com) translates a user-supplied input into a 16 bit, SPI-compatible data stream that programs  $IC_1$ 's output frequency. The LTC6903's output frequency depends on two control coefficients,

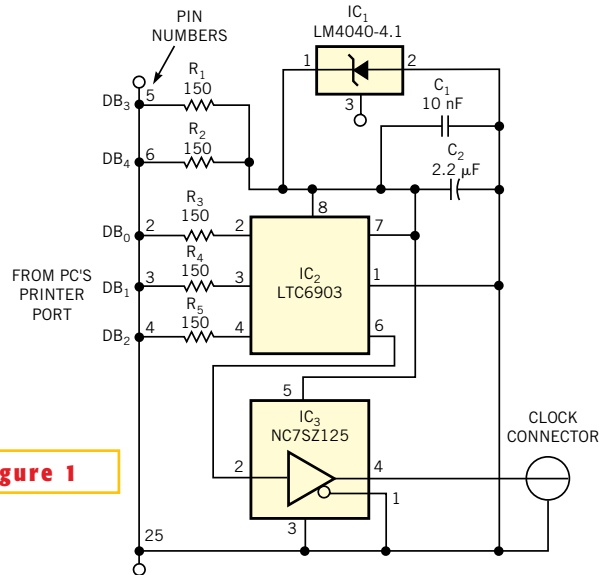

**Figure 1**

PC-programmable wide-range clock source features minimal component count.

OCT and DAC. The program derives the closest values for OCT and DAC by solving the equation:  $f = (2^{OCT}) \times 2078 / (2 - (DAC) / 1024)$ . At initial application of power,  $IC_2$ 's output frequency defaults to 1.039 kHz. □


# Constant-on-time buck-boost regulator converts a positive input to a negative output

Robert Bell, National Semiconductor Inc, Chandler, AZ

**B**UCK REGULATORS find wide application as step-down regulators for converting large positive input voltages into a smaller positive output voltage. **Figure 1** shows a simplified buck regulator that operates in continuous-conduction mode—that is, the inductor current always remains positive. The output voltage,  $V_{OUT}$ , is equal to  $D \times V_{IN}$ , where  $D$  is the duty-cycle ratio of the buck switch,  $Q_1$ , and  $V_{IN}$  is the input voltage. The duty cycle,  $D$ , is equal to  $T_{ON}/T_S$ , where  $T_{ON}$  is the on-time of  $Q_1$  and  $T_S$  is the switching-frequency period.

You can reconfigure a buck regulator into a buck-boost circuit to convert a positive voltage into a negative voltage (**Figure 2**). The basic component configurations of both circuits are similar, and the inductor and the rectifier diode are transposed. Because the main switch,  $Q_1$ , remains in the same location for both configurations, you can use an IC buck regulator for either topology. Switching on  $Q_1$  applies input voltage  $V_{IN}$  across power inductor  $L_1$ , and current in the inductor ramps up while  $Q_1$  remains on. When  $Q_1$  switches off, inductor current continues to flow through  $C_1$ , the load resistance and  $D_1$ , producing a negative output voltage. During  $Q_1$ 's next on-time interval, the output capacitor supplies current to the load.

**Figure 3** shows a low-cost buck-boost converter based on the LM5010 buck-

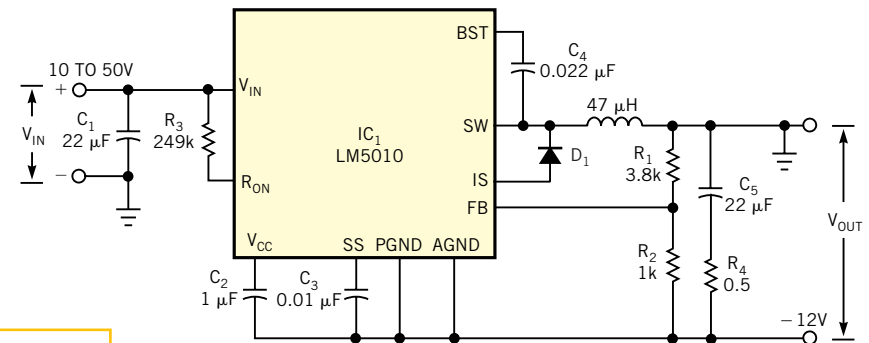

**Figure 3**

Based on National Semiconductor's LM5010, this buck-boost regulator operates over a wide input-voltage range.

regulator IC that converts a 10 to 50V positive supply voltage into  $-12V$ . Although many applications use a fixed switching frequency and modulate the output pulse width, this design features a constant-on-time approach in which the IC's internal output transistor turns on for an interval that's inversely proportional to the difference between the circuit's input and output voltage.


Inside  $IC_1$ , a regulation comparator monitors the output voltage from voltage divider  $R_1$  and  $R_2$  and a 2.5V internal reference, and, if the output voltage falls below the desired value, the comparator switches on  $IC_1$ 's output transistor for an interval that an on-timer determines:

$$T_{ON} = K \times \frac{R_{ON}}{V_{IN} + V_{OUT}}$$

where  $K$  represents a constant,  $R_3$  sets the buck switch's on-time interval,  $V_{IN}$  is the input voltage, and  $V_{OUT}$  is the magnitude of the output voltage. Substitute  $T_{ON} = 1/F_S$  and then solve for  $F_S$  to yield:


$$F_S = \frac{V_{OUT}}{K \times R_{ON}}$$

Providing that current through  $L_1$  remains continuous,  $V_{OUT}$  remains regulated. Because  $R_3$  and  $K$  are constants, switching frequency  $F_S$  remains constant. This relationship holds true provided that the current through the inductor remains continuous. At lighter loading, the current in the inductor becomes discontinuous—that is, the inductor current drops to zero for a portion of the switching cycle. At the onset of discontinuous operation, the

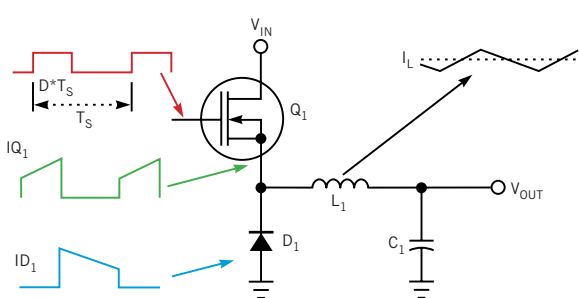

**Figure 1**

In the basic buck-regulator circuit, current flows continuously through inductor  $L_1$ .

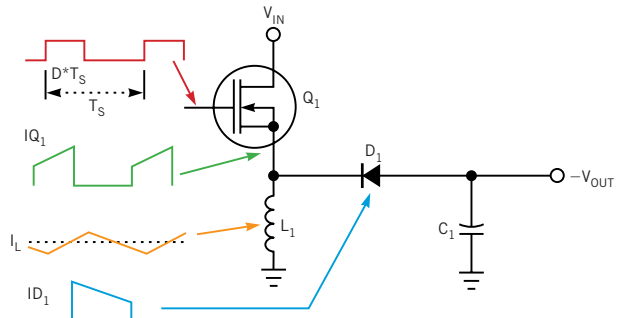

**Figure 2**

The buck-boost regulator circuit produces a negative output voltage.

switching frequency begins to drop and thus brings  $V_{OUT}$  back into regulation.

Operating a buck-boost regulator in fixed-frequency mode without an oscillator eliminates loop compensation and stabilization components and, as a bonus, offers fast transient response unlimited by feedback-network lag time. With the component values in **Figure 3**, the regulator operates at approximately

400 kHz, delivering 12V at approximately 0.5A for 10V input and approximately 1A of output current for 50V input. Resistor  $R_4$  ensures that the minimum amount of output-ripple voltage necessary for regulation—approximately 25 mV—is available.

Fixed-frequency operation without an oscillator offers a low-cost, easily implemented regulator with no loop-compen-

sation or stability issues to worry about. The transient response is fast, because there are no bandwidth-limiting feedback components. The regulator operates at approximately 400 kHz. The output-current capability varies with the input voltage. When you apply 10V input voltage, the output-current capability is approximately 0.5A, and, at 50V input, the output current is approximately 1A. □


## Rainbow LED indicates voltage with color

David Prutchi, Impulse Dynamics, Haifa, Israel

**M**ETERS THAT INDICATE analog levels via a moving-pointer meter, a numeric display, or a column of LEDs typically occupy considerable panel area and require more than a casual glance to read. An indicator lamp or LED takes little space but indicates only an on or off condition. However, an unobtrusive LED that changes color as a function of a measured value would enable an observer to easily assess the measurement.


The circuit in **Figure 1** comprises  $IC_1$ , a Microchip PIC12F675 microcontroller driving  $IC_2$ , a Kingbright AAF5060PBESEEVG “rainbow” indicator that contains three ultrabright LED chips (red, green, and blue) within one package. Modulating each LED’s duty cycle produces all of the perceivable colors of the visible spectrum, including white light. **Listing 1** at the Web version of this Design Idea at [www.edn.com](http://www.edn.com) contains a PIC program for the PicBasic Pro compiler, which is available from MicroEngineering Labs Inc ([www.melabs.com](http://www.melabs.com)). This program converts a 0 to 5V input applied to Pin 3 of  $IC_1$  to an 8-bit digital value that corresponds to a perceived color containing certain amounts of red, blue, and green.

Under control of a PWM routine, each LED flashes for an interval proportional to its corresponding content of red, green, or blue. During each PWM frame, an LED die receives power for as many as 14 steps per frame as the color map of **Figure 2** shows. (You can view the color map at the Web version of this Design Idea at [www.edn.com](http://www.edn.com).) Although not all LEDs are necessarily simultaneously illuminat-

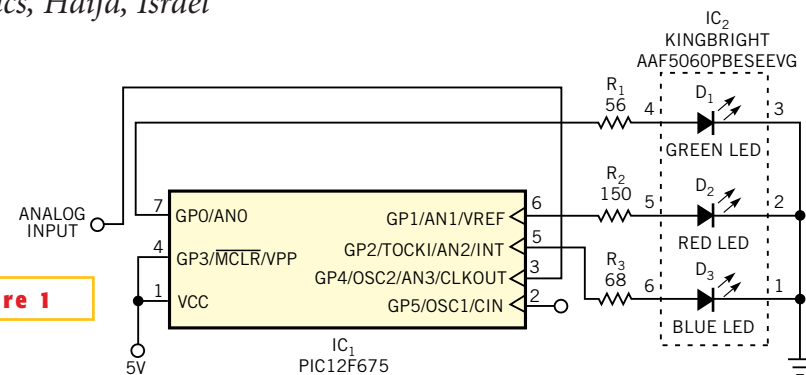

**Figure 1**

Using a minimal number of components, this voltage-to-color converter uses a single rainbow LED to monitor an analog voltage level.

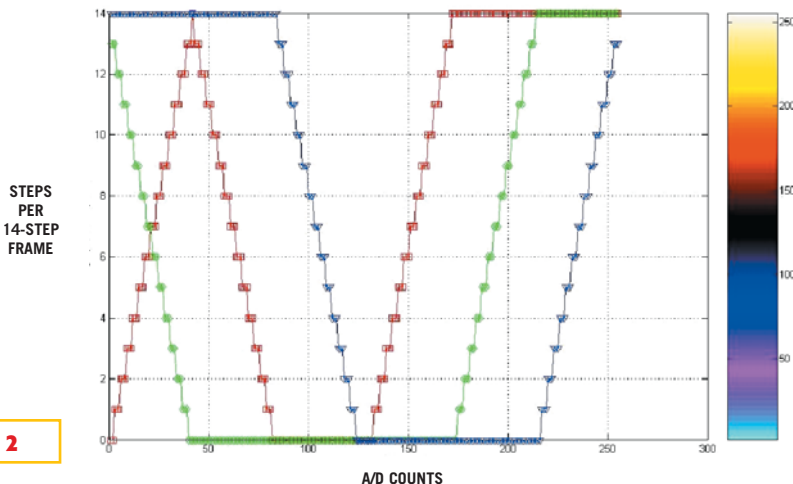

**Figure 2**

You can alter the color versus input-voltage palette by modifying the firmware.

ed, the eye’s slow response integrates their output to create the illusion of a change in intensity proportional to the duty cycle. The RGB-encoding function in **Listing 1** assumes that the analog input to  $IC_1$  has a zero-signal offset of 2.5V, which switches all LEDs off. “Cool” colors

(shades of blue, purple, and aqua) denote an input in the 0 to 2.5V range, and “hot” colors (shades of red, orange, yellow, and white) denote an input in the 2.5 to 5V range. You can create different palettes by changing the primary-color proportions stored in the RGB encoding table. □